

EE3007D Power Electronics

Course Project Report

Buck Boost Converter

Aim

To develop a Buck Boost Converter that can convert a 15V dc input to 10V and 25V dc outputs at 25W

Apparatus Used


- | | |
|---------------------------------------|---------|
| 1. TLP250 Optocoupler | - 1 Nos |
| 2. 1000uF, 63V Electrolytic Capacitor | - 1 Nos |
| 3. Inductor wound for 8.34mH | - 1 Nos |
| 4. 10W, 100E Resistor Bank | - 4 Nos |
| 5. IRF540 Power MOSFET | - 1 Nos |
| 6. 1N5048 Power Diode | - 1 Nos |

Design


- Theoretical Duty Cycles for 10V and 25V dc outputs are 0.4 and 0.625 respectively
- The minimum inductance so that the circuit does not enter discontinuous conduction mode(considering the worst case) was found to be 3.125mH. Accordingly, an inductor of inductance 8.34mH was wound.

- The minimum value of capacitor was designed to be 250 microF.
.Accordingly a 1000microF ,63V capacitor was used.
- Four resistor banks of rating 100 ohm 10W were connected parallel inorder to obtain a total resistance of 25 ohm 50W.


Simulation:

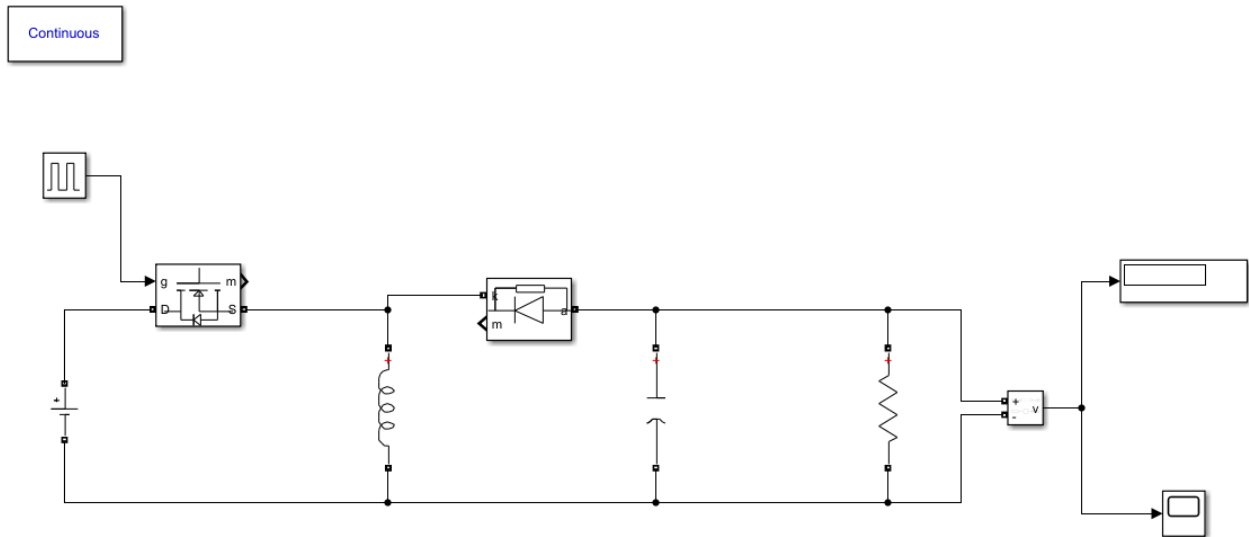


BUCK OUTPUT VOLTAGE:

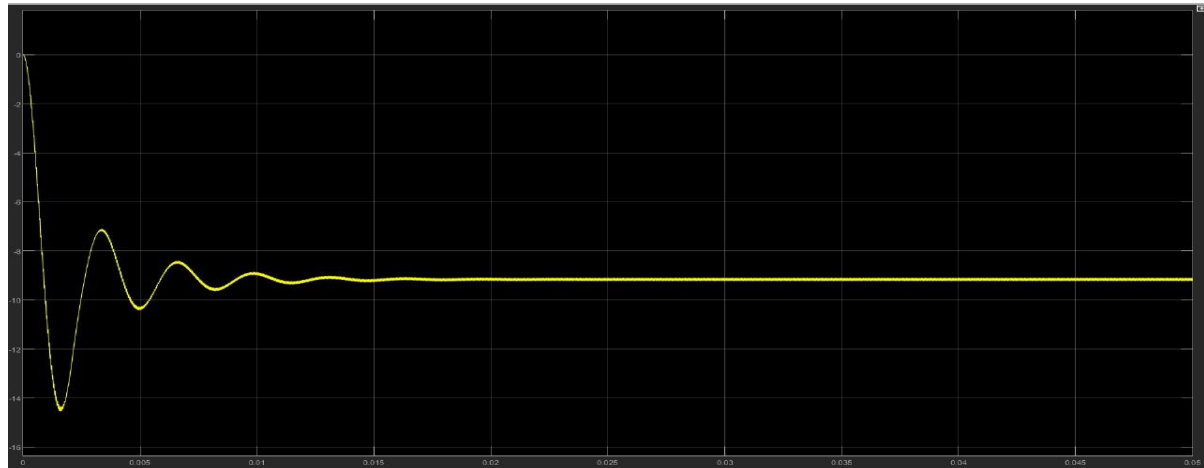


BUCK INDUCTOR CURRENT:

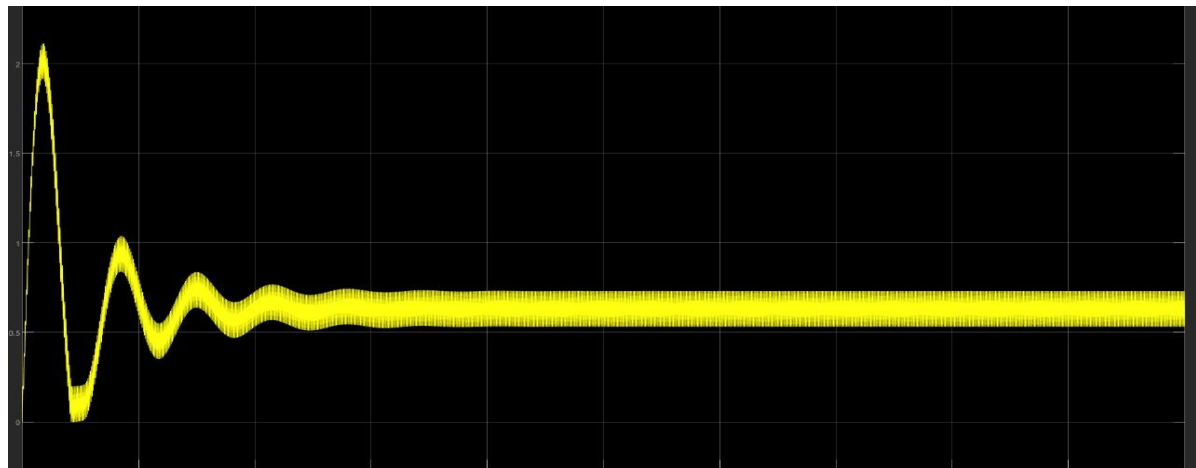



BOOST OUTPUT VOLTAGE:

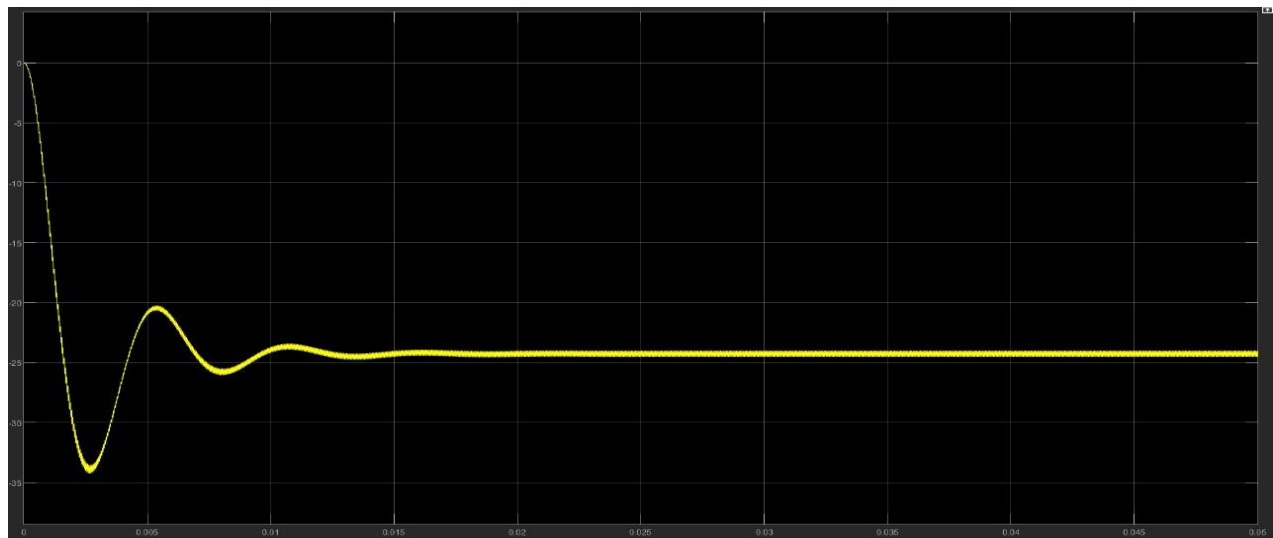

BOOST INDUCTOR CURRENT:

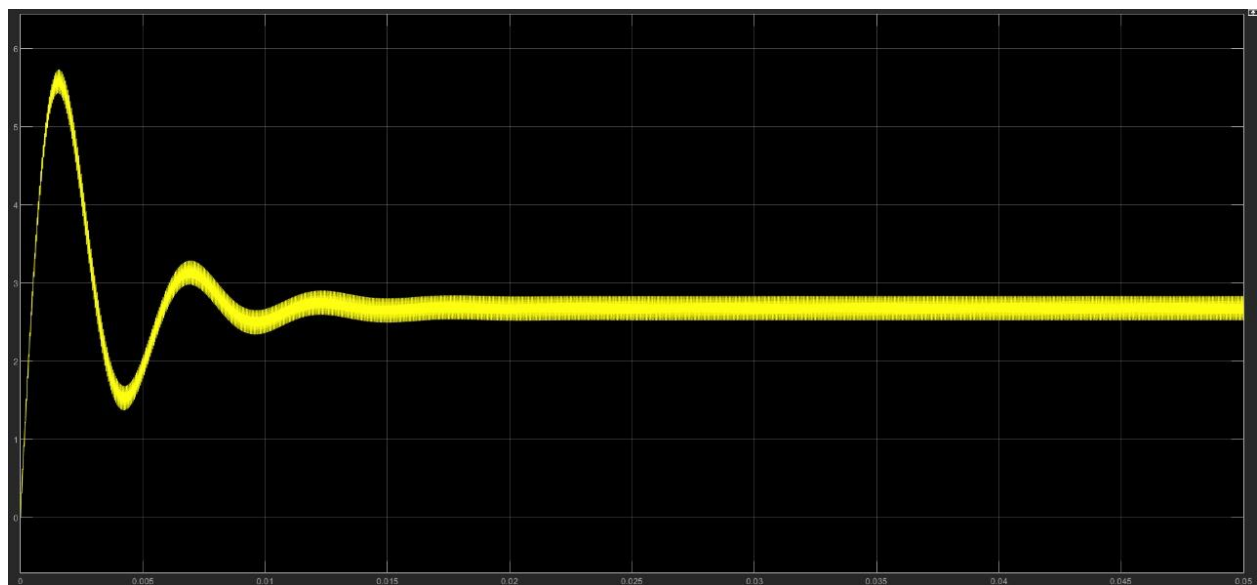

Hardware:

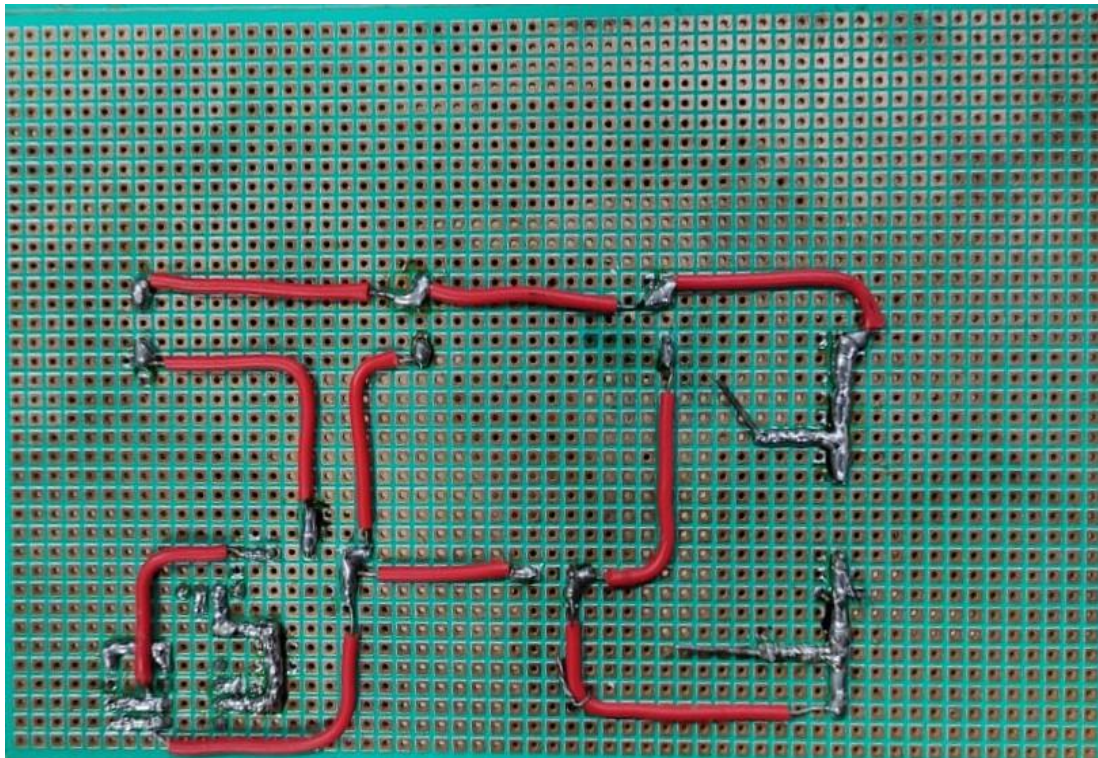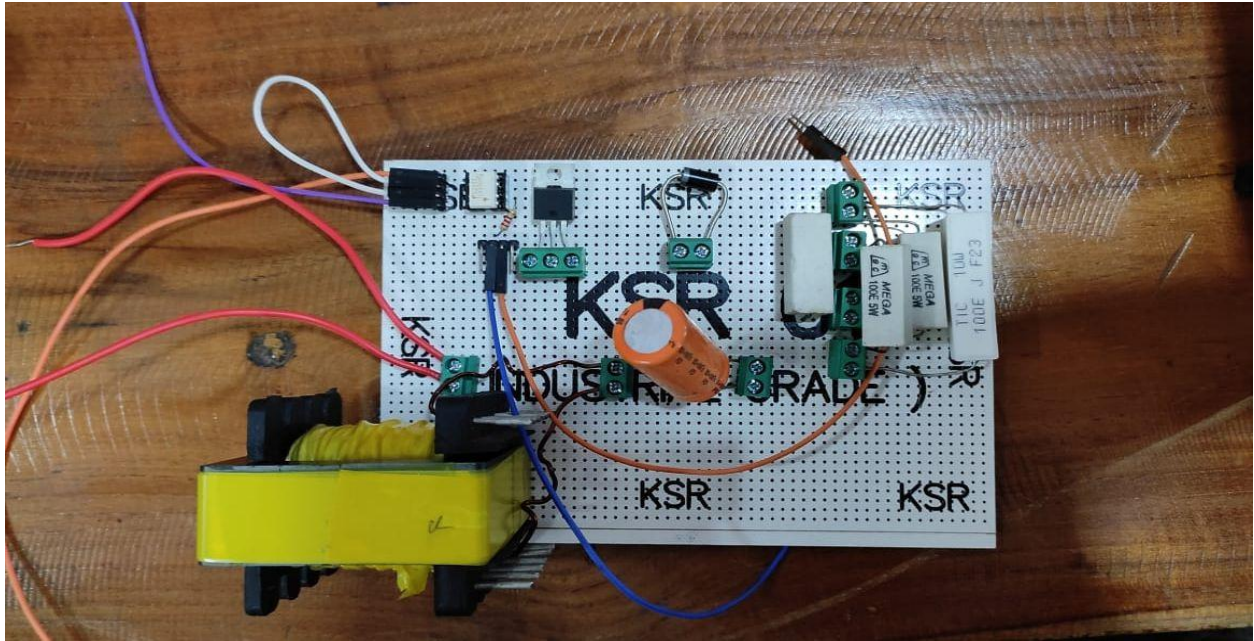

Result:

The buck-boost converter design met the specified requirements, providing a stable 10V output over the input voltage of 15 V (Buck converter) and a stable 24V output over the input of 15 V (Boost converter)

Submitted by

Mehna A S :B210808EE

Lukman Nazir :B210870EE

Madhav Menon: B210821EE

Neeraj S :B210879EE

